




JOINT INSTITUTE
交大密西根学院

ECE2700J SU23 RC3

Logic Optimization, K-map

Wenyue Li
6/3/2024

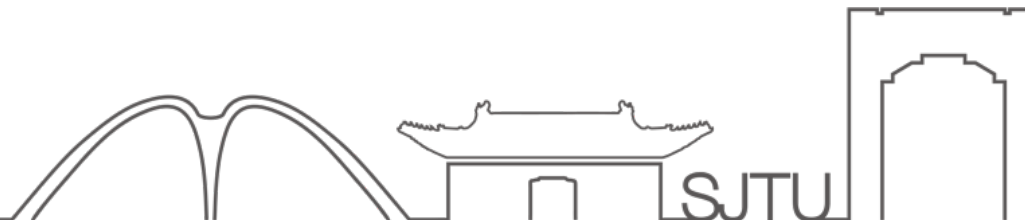


JOINT INSTITUTE
交大密西根学院

Logic Optimization

Simplification and Optimization

Intention : design a **better** circuit

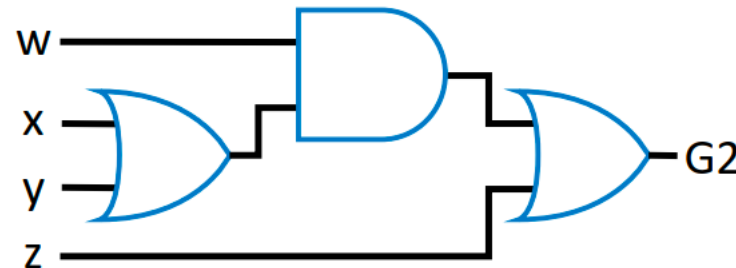
- Delay – the time from input change to correct stable output response
 - Every gate has delay of “1 gate-delay”, the gate delay of a circuit is judged by its critical path
- Size – the number of transistors
 - Every gate input requires 2 transistors
 - Ignore inverters for simplicity
- Sacrifices delay for smaller size



Logic Optimization

Simplification and Optimization

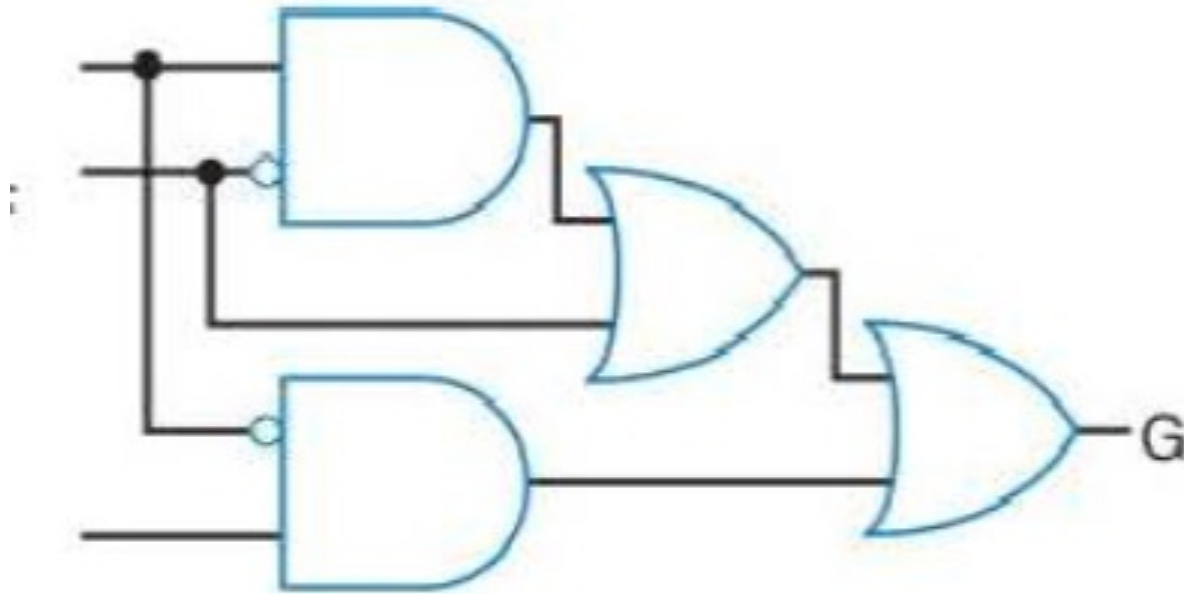Exercise: find the sizes and Delay of the following circuit



Logic Optimization

Simplification and Optimization

Exercise: Optimize the circuit with the equation shown below. Write its original size and delay and the optimized sizes and delay.

$$F = xyz + xyz' + x'y'z' + x'y'z$$

K-map

K-map

- A graphical technique used to simplify a logic equation
- A way to show the relationship between the logic inputs and corresponding output
 - Like truth table
- Much cleaner and more procedural than algebraic simplification by theorems of Boolean algebra.
- Theoretically, it can be used for any number of input variables,
 - BUT is only practical for less than six, we will limit our discussion to logic equations with five or less variables

K-map

How to draw K-map

- K-map can be filled up directly from a truth table
 - Each minterm corresponds to a cell in the K-map
- K-map cells are labeled so that both horizontal and vertical movement differ only in one variable

F		Y	
		Y'	Y
X			
X'		m0	m1
X		m2	m3

F		YZ			
		Y'Z'	Y'Z	YZ	YZ'
X					
X'		m0	m1	m3	m2
X		m4	m5	m7	m6

F		YZ			
		Y'Z'	Y'Z	YZ	YZ'
WX					
W'X'		m0	m1	m3	m2
W'X		m4	m5	m7	m6
WX		m12	m13	m15	m14
WX'		m8	m9	m11	m10

K-map

Basic knowledge of K-map

Label the Rows and Columns by 0 and 1

F WX \ YZ		YZ	Y'Z'	Y'Z	YZ	YZ'
		00	01	11	10	
W'X' 00	1	0	1	1		
W'X 01	0	0	1	0		
WX 11	1	0	1	0		
WX' 10	1	1	0	0		

We can write a equation from K-map similar to truth table.

F=

K-map

Grouping and Cancelling

Why we need to group?

		Y	
		0	1
X	0	1	0
	1	0	0

$X'Y'$

		Y	
		0	1
X	0	1	1
	1	0	0

X'

K-map

Grouping and Cancelling

Grouping rules

- No zeros in the group

A 2x4 K-map with variables F, YZ, and X. The map contains 1s at (0,01), (0,11), (1,01), and (1,11). A group of four 1s is circled in black, and the entire map is crossed out with a large red X.

F \ YZ \ X	00	01	11	10
0	0	1	1	0
1	0	0	1	0

A 2x4 K-map with variables F, YZ, and X. The map contains 1s at (0,01), (0,11), (1,01), and (1,11). Two groups of two 1s each are circled: one in red (horizontal group at X=0) and one in blue (vertical group at YZ=11).

F \ YZ \ X	00	01	11	10
0	0	1	1	0
1	0	0	1	0

- Group as many adjacent 1's as possible

A 4x4 K-map with variables F, YZ, and WX. The map contains 1s at (00,00), (00,01), (00,11), (00,10), (01,00), (01,01), (01,11), (01,10), (11,01), and (11,11). A group of eight 1s is circled in red (the entire top half of the map), and a group of two 1s is circled in black (the 1s at (11,01) and (11,11)).

F \ YZ \ WX	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	0	1	0
10	1	0	0	0

- Edges wrap around

A 2x4 K-map with variables F, YZ, and X. The map contains 1s at (0,00), (0,01), and (0,11). A group of three 1s is circled in black, and the entire map is crossed out with a large red X.

F \ YZ \ X	00	01	11	10
0	1	1	1	0
1	0	0	0	0

A 2x4 K-map with variables F, YZ, and X. The map contains 1s at (0,00), (0,01), and (0,11). Two groups of two 1s each are circled: one in red (horizontal group at X=0) and one in blue (horizontal group at X=0).

F \ YZ \ X	00	01	11	10
0	1	1	1	0
1	0	0	0	0


A 2x4 K-map with variables F, YZ, and X. The map contains 1s at (0,00), (0,10), (1,00), and (1,10). Two groups of two 1s each are circled in red: one horizontal group at X=0 and one horizontal group at X=1.

F \ YZ \ X	00	01	11	10
0	1	0	0	1
1	1	0	0	1

K-map

Grouping and Cancelling

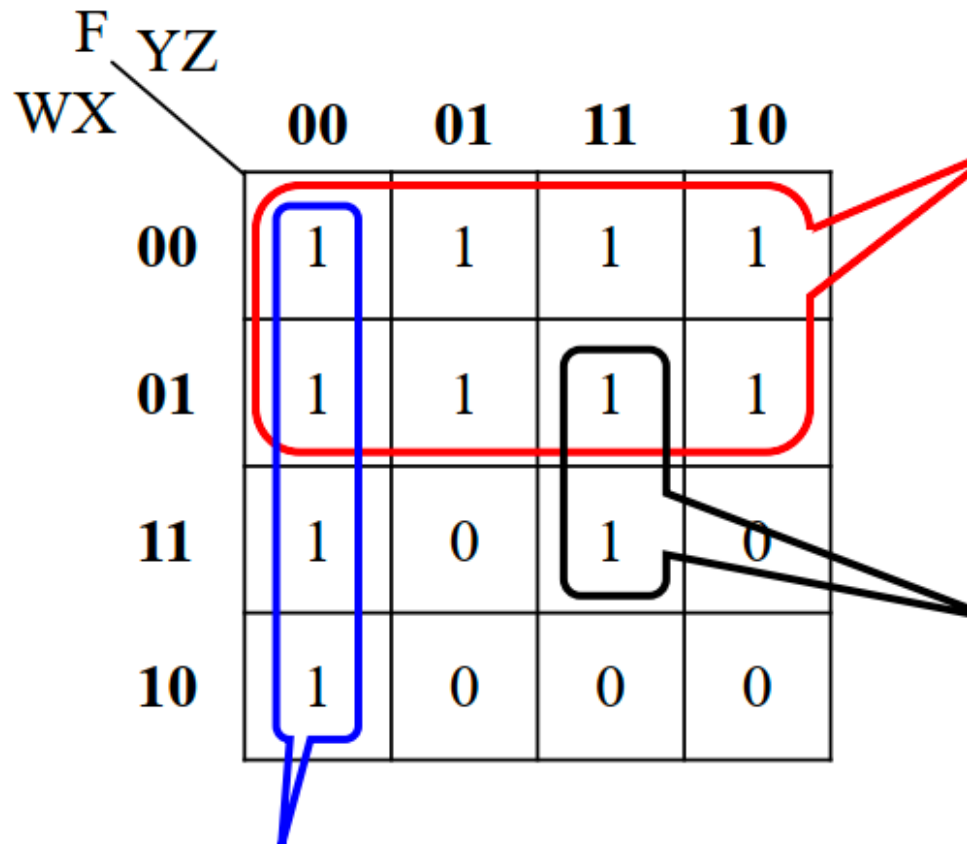How to quickly use group to simplify a circuit?



K-map

Grouping and Cancelling

Exercise: Quickly write the equation of the circled groups.

	00	01	11	10
00	0	1	0	1
01	1	0	0	1
11	0	0	0	0
10	0	1	0	1

Diagram showing a 4x4 K-map with groupings: a blue vertical group of 1s in column 01, a red vertical group of 1s in column 10, and a black horizontal group of 1s in row 01.

	00	01	11	10
00	1	1	1	1
01	1	0	0	0
11	1	1	1	1
10	1	0	0	0

Diagram showing a 4x4 K-map with groupings: a red horizontal group of 1s in row 00, a black horizontal group of 1s in row 11, and a blue vertical group of 1s in column 00.

K-map

Prime Implicants

- Implicant: is a product term
- A prime implicant (PI) is a group that cannot be entirely contained by another implicant

F YZ WX		YZ			
		00	01	11	10
WX	00	1	1	1	1
	01	1	1	1	1
	11	0	0	0	0
	10	0	0	0	0

— Prime implicant

..... Not prime implicants

F YZ		WX			
		00	01	11	10
ts	00	1	1	1	0
	01	0	0	1	0
	11	0	0	0	0
	10	0	0	0	1

K-map

Prime Implicant

Exercise: Find all PIs in the following K-map

F WX \ YZ		YZ			
		00	01	11	10
WX	00	1	0	1	1
	01	0	1	1	0
	11	0	1	1	0
	10	1	1	1	1

K-map

Essential Prime Implicant

- A prime implicant (PI) is essential if a cell is covered ONLY by that PI
- The essential PIs can be found by
 - looking at each cell marked as 1 and not covered by any other essential PI
 - and checking the number of PIs that cover it

F WX \ YZ		YZ			
		00	01	11	10
WX	00	1	0	1	1
	01	0	1	1	0
	11	0	1	1	0
	10	1	1	1	1

K-map

Essential Prime Implicant

- Essential PIs **have to be used in the simplified equation**
- Cells not covered by essential PIs can be represented by any PIs

covering them

F		YZ			
WX		00	01	11	10
00	1	0	1	1	
01	0	1	1	0	
11	0	1	1	0	
10	1	1	1	1	

K-map

Don't care conditions in K-map

- The possible input combinations might not be all valid or not for consideration for a device
 - Hence we don't care what the corresponding outputs are under those conditions
 - Called **don't care** conditions
 - Mark the corresponding outputs by **X**

A	B	C	D	F
<i>0</i>	<i>0</i>	<i>0</i>	<i>0</i>	<i>X</i>
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
<i>1</i>	<i>0</i>	<i>0</i>	<i>1</i>	<i>X</i>
1	0	1	0	1
1	0	1	1	1
<i>1</i>	<i>1</i>	<i>0</i>	<i>0</i>	<i>X</i>
<i>1</i>	<i>1</i>	<i>0</i>	<i>1</i>	<i>X</i>
<i>1</i>	<i>1</i>	<i>1</i>	<i>0</i>	<i>X</i>
1	1	1	1	1